


#### 4. General Lab Score

##### Section 5.1

- Resistance/ inductance measurements.

|                                  |                            |
|----------------------------------|----------------------------|
| $R_1: 100 \Omega$                | $98.1 \pm 0.1 \Omega$      |
| $R_2: 330 \Omega$                | $321.1 \pm 0.2 \Omega$     |
| L: 150 mH Inductance             | $146.9 \pm 0.1 \text{ mH}$ |
| $R_L: 150 \text{ mH Resistance}$ | $166.0 \pm 0.2 \Omega$     |

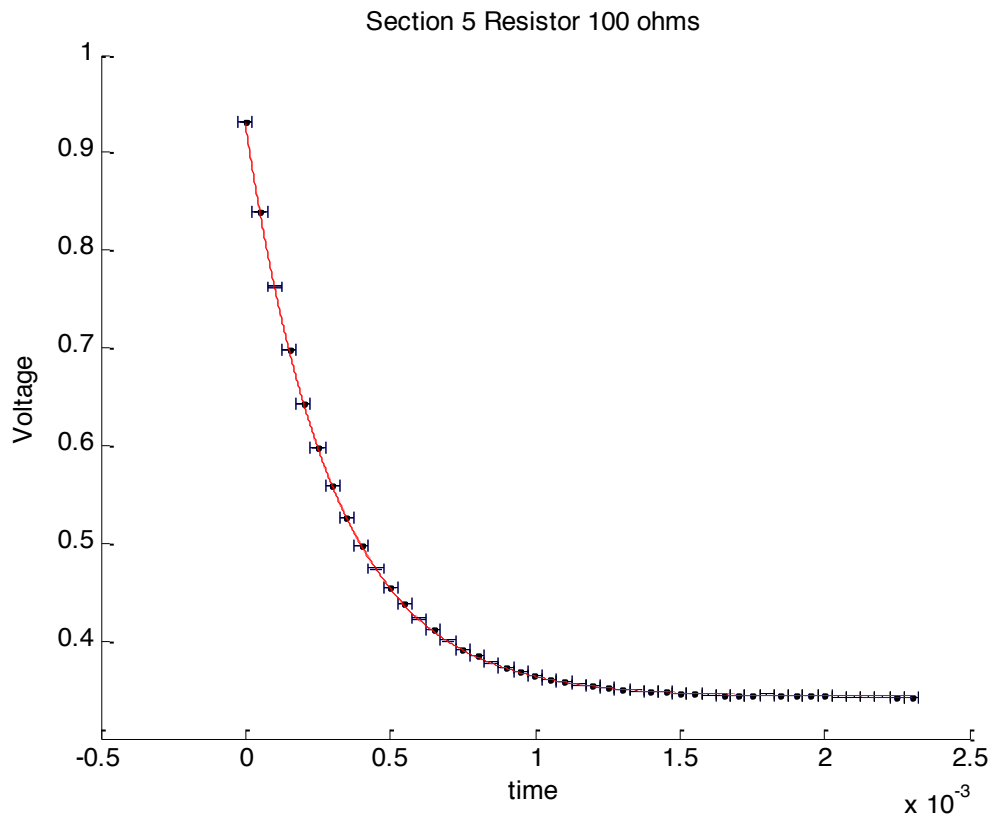- Voltage-time plots with fits (refer to Datstudio guide for fitting).



Enter Approximation of Noise Voltage Error: 0.0002393

Enter estimate for parameter A: 0.70

Enter estimate for parameter tau: 0.000225


Enter estimate for parameter B: 0.3364

Parameter A =  $5.873071\text{e-}01 \pm 3.901827\text{e-}04$

Parameter tau =  $3.003718\text{e-}04 \pm 3.751937\text{e-}07$

Parameter B =  $3.427218\text{e-}01 \pm 1.160282\text{e-}04$

Section 5 Resistor 330 ohms

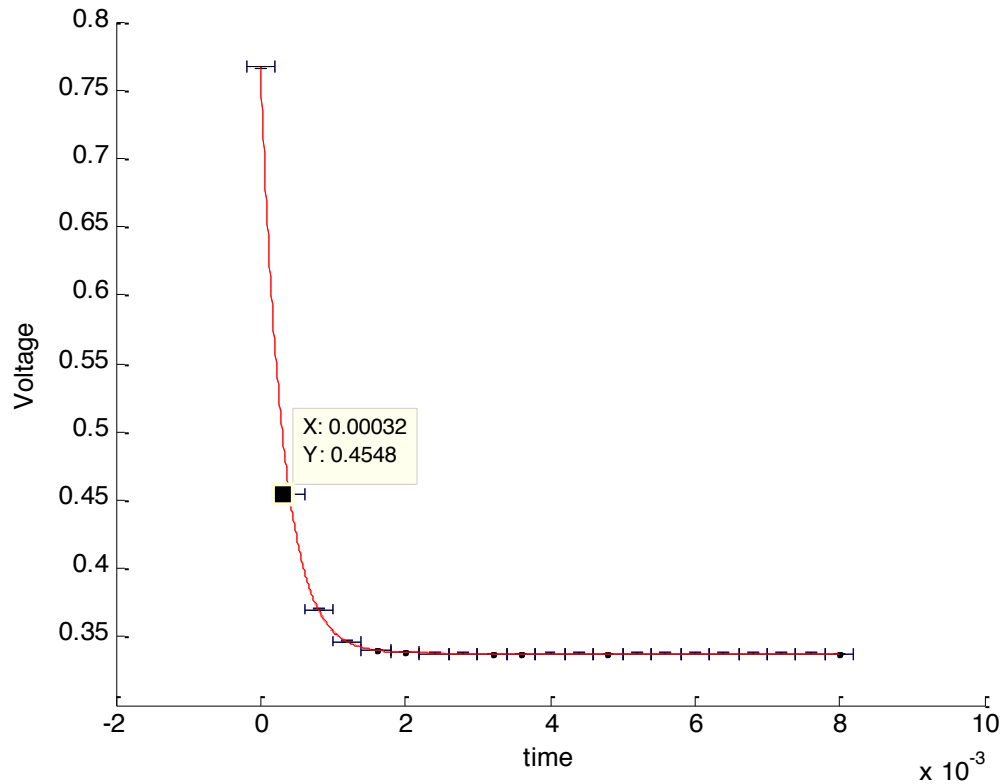

Enter Approximation of Noise Voltage Error: 0.000249

Enter estimate for parameter A: 0.4292

Enter estimate for parameter tau: 0.00029

Enter estimate for parameter B: 0.3376

Parameter A = 4.287834e-01 +/- 2.379071e-04

Parameter tau = 3.081195e-04 +/- 4.409319e-07

Parameter B = 3.377801e-01 +/- 5.567916e-05

- Model function with parameters

Resistor 110 Ω:

Model function:

$$f(x) = 0.5873 \times e^{\frac{-x}{0.000308}} + 0.3427$$

Fitted Parameters:

Parameter A: 0.5873± 0.0004

Parameter tau: 0.000300±0.000001

Parameter B: 0.3427±0.0001

Resistor 330 Ω:

Model function:

$$f(x) = 0.4288 \times e^{\frac{-x}{0.0003}} + 0.338$$

Fitted Parameter:

Parameter A: 0.4288± 0.0004

Parameter tau: 0.000308±0.000001


Parameter B:  $0.3378 \pm 0.0001$

**Section 7.**

- Resistance/ inductance measurements.

|                          | With Iron Core          | Without Iron Core   |
|--------------------------|-------------------------|---------------------|
| Time constant            | $0.000510 \pm 0.000006$ | $0.0027 \pm 0.0001$ |
| Resistor ( $330\Omega$ ) | $323.7 \pm 5.5$         | $323.7 \pm 5.5$     |
| Resistance(In)           | $5.5 \pm 0.1$           | $5.5 \pm 0.1$       |
| Resistance (tot)         | $329.2 \pm 0.2$         | $329.2 \pm 0.2$     |
| Inductance (In)          | $21.1 \pm 0.1$          | $8.1 \pm 0.1$       |

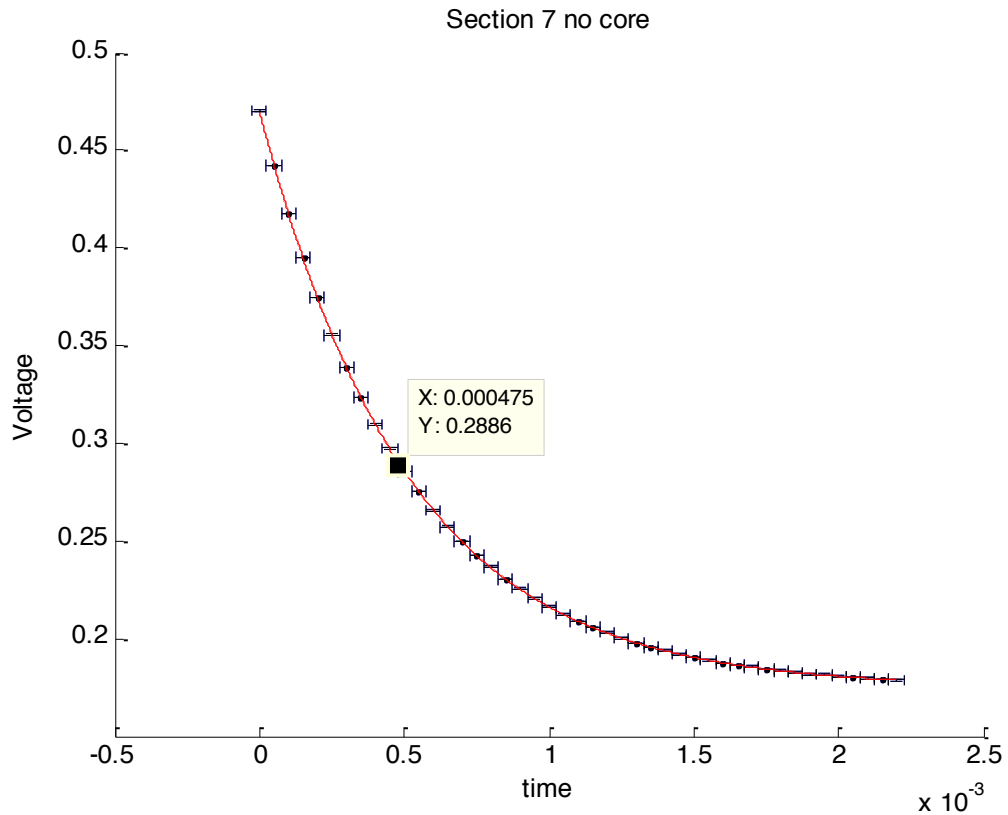- Voltage-time plots with fits (refer to Datastudio guide for fitting).



Enter Approximation of Noise Voltage Error: 0.00024

Enter estimate for parameter A: 0.2942


Enter estimate for parameter tau: 0.000475

Enter estimate for parameter B: 0.1789

Parameter A =  $2.952971e-01 \pm 1.027026e-04$

Parameter tau =  $5.103676e-04 \pm 4.327959e-07$

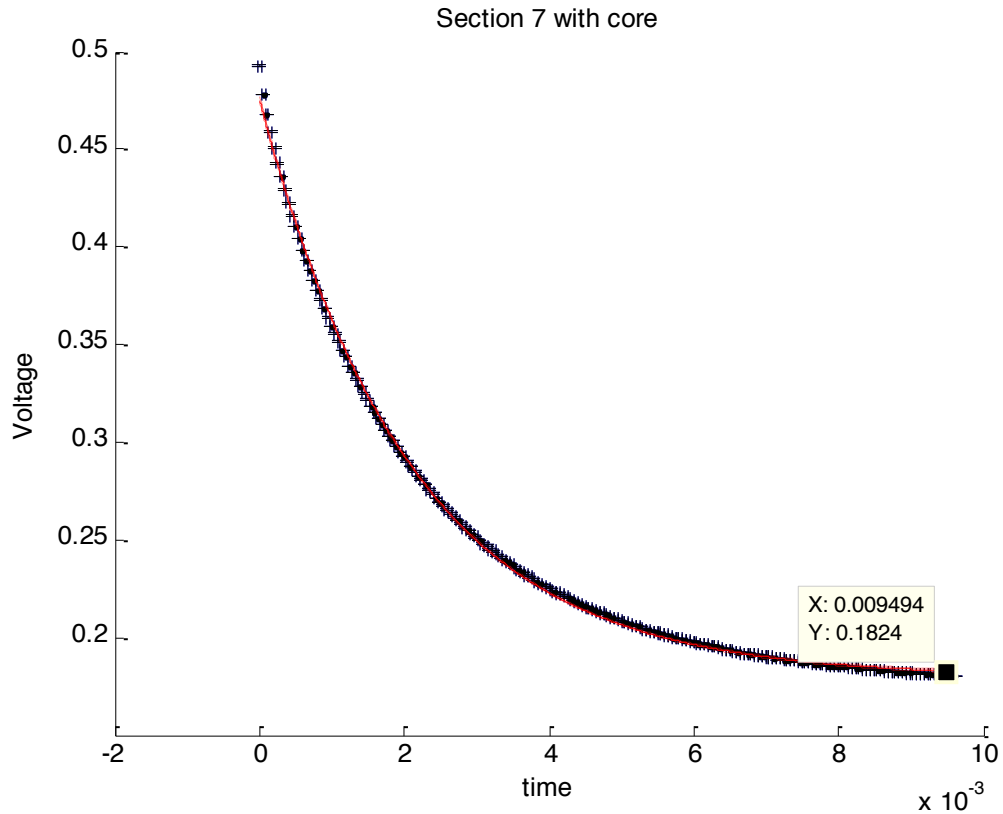Parameter B =  $1.747968e-01 \pm 5.885074e-05$



Enter Approximation of Noise Voltage Error: 0.00021

Enter estimate for parameter A: 0.3125

Enter estimate for parameter tau: 0.002

Enter estimate for parameter B: 0.1804

Parameter A = 2.954865e-01 +/- 7.010088e-04

Parameter tau = 2.081141e-03 +/- 1.131808e-05

Parameter B = 1.799013e-01 +/- 3.500620e-04

- Model function and fitted parameters

No core:

Model function:

$$f(x) = 0.2953 \times e^{\frac{-x}{0.000510}} + 0.1758$$

Fitted Parameter:

Parameter A: 0.2953 ± 0.0001

Parameter tau: 0.000510 ± 0.000001

Parameter B: 0.1758 ± 0.0001

With core:

Model function

$$f(x) = 0.2953 \times e^{\frac{-x}{0.000510}} + 0.1758$$

Fitted Parameter:

Parameter A: 0.2955 ± 0.0007

Parameter tau: 0.00208±0.00001  
Parameter B: 0.1799 ±0.0003

## 5. Analysis Section 5.1

- Determine the resistance ratio:  $\frac{R_{tot,1}}{R_{tot,2}}$  and uncertainty.

$$\frac{R_{tot,1}}{R_{tot,2}} = \frac{R_L + R_1}{R_L + R_2} = 0.542$$

Error of propagation:

$$\partial R_{tot,1} = \sqrt{\partial R_L^2 + \partial R_1^2} = 0.2$$

$$\partial R_{tot,2} = \sqrt{\partial R_L^2 + \partial R_2^2} = 0.3$$

$$\partial \frac{R_{tot,1}}{R_{tot,2}} = \partial R_{rat} = \sqrt{\left(\frac{\partial R_{rat}}{\partial R_1} \partial R_1\right)^2 + \left(\frac{\partial R_{rat}}{\partial R_2} \partial R_2\right)^2} = 0.006$$

$$\text{Ans} = 0.542 \pm 0.006$$

- Determine measured  $\tau$ 's and uncertainties from fitted parameters.  
Expected  $\tau$  (from Eq 5):

$$\tau_1 = \frac{L}{R_{tot,1}} = \frac{0.1469}{264.1} = 0.000556$$

Error of Propagation:

$$\partial \tau_1 = \sqrt{\left(\frac{\partial \tau_1}{\partial L} \partial L\right)^2 + \left(\frac{\partial \tau_1}{\partial R} \partial R\right)^2} = 0.000008$$

$$\tau_1 = 0.000556 \pm 0.000008$$

$$\tau_2 = \frac{L}{R_{tot,2}} = \frac{0.1469}{487.1} = 0.000301$$

Error of Propagation:

$$\partial \tau_2 = \sqrt{\left(\frac{\partial \tau_2}{\partial L} \partial L\right)^2 + \left(\frac{\partial \tau_2}{\partial R} \partial R\right)^2} = 0.000011$$

$$\tau_2 = 0.000301 \pm 0.000011$$

Measured  $\tau$ 's from fitted parameters

$$\tau_1 = 0.000300 \pm 0.000001$$

$$\tau_2 = 0.000308 \pm 0.000001$$

- Determine  $\tau$  ratio:  $\frac{\tau_1}{\tau_2}$  and uncertainty.

$$\text{Expected } \frac{\tau_1}{\tau_2} = 1.847$$

Error of Propagation:

$$\partial \frac{\tau_1}{\tau_2} = \partial \tau_{ratio} = \sqrt{\left(\frac{\partial \tau_{rat}}{\tau_1} \partial \tau_1\right)^2 + \left(\frac{\partial \tau_{rat}}{\tau_2} \partial \tau_2\right)^2} = 0.073$$

$$\text{Expected } \frac{\tau_1}{\tau_2} = 1.847 \pm 0.073$$

$$\text{Measured } \frac{\tau_1}{\tau_2} = 0.974$$

Error of propagation:

$$\partial \frac{\tau_1}{\tau_2} = \partial \tau_{ratio} = \sqrt{\left(\frac{\partial \tau_{rat}}{\tau_1} \partial \tau_1\right)^2 + \left(\frac{\partial \tau_{rat}}{\tau_2} \partial \tau_2\right)^2} = 0.004$$

$$\text{Measured } \frac{\tau_1}{\tau_2} = 0.974 \pm 0.004$$

- Given  $L$  is fixed, show the relationship between these ratios. Verify this with a quantitative comparison. *Does  $\tau$ 's dependence on  $R$  agree with Eq. 5?*

$$L = \tau R \text{ so } \frac{\tau_1}{R_{tot,2}} = \frac{\tau_2}{R_{tot,1}} \text{ hence } \frac{\tau_1}{\tau_2} = \frac{R_{tot,2}}{R_{tot,1}}$$

$$\text{Expected } \frac{\tau_1}{\tau_2} = 1.847 \pm 0.073$$

$$\frac{R_{tot,2}}{R_{tot,1}} = 1.845 \pm 0.002$$

Percentage Error:

$$\frac{|Theoretical - Experimental|}{Experimental} \times 100\%$$

$$\frac{\left| \text{Expected } \frac{\tau_1}{\tau_2} - \frac{R_{tot,2}}{R_{tot,1}} \right|}{\frac{R_{tot,2}}{R_{tot,1}}} \times 100\% = 0.1\%$$

T-test:

$$t = \frac{\bar{x}_1 - \bar{x}_2}{\sqrt{\frac{S_1^2}{N_1} + \frac{S_2^2}{N_2}}}$$

where

$\bar{x}_1$  = mean value of Experimental Value

$\bar{x}_2$  = mean value of Theoretical Value

$S_1$  = Standard deviation of Experimental Value

$S_2$  = Standard deviation of Theoretical Value

$N_1$  = Number of data in Experimental Value

$N_2$  = Number of data in Theoretical Value

In this case,

$$\bar{x}_1 = 1.845$$

$$\bar{x}_2 = 1.847$$

$$S_1 = 0.006$$

$$S_2 = 0.073$$

$$N_1 = 1$$

$$N_2 = 1$$

$$t\text{-value} = -0.027$$

|                  |         |
|------------------|---------|
| Percentage error | t-value |
| 0.1%             | 0.027   |

Yes,  $\tau$ 's dependence on R agree with Eq(5).

- With knowledge of the circuit's total resistance determine the inductance value of the inductor; *does it agree with the labeled value (quant. Compare)?*

|            | $\tau$            | $R$           | $L$           |
|------------|-------------------|---------------|---------------|
| Resistor 1 | 0.000300±0.000001 | 264.1 ± 0.2 Ω | 0.0792±0.0002 |
| Resistor 2 | 0.000308±0.000001 | 487.1 ± 0.3 Ω | 0.1500±0.0005 |

|          |       |       |               |
|----------|-------|-------|---------------|
| Expected | ----- | ----- | 0.1469±0.0001 |
|----------|-------|-------|---------------|

|               |              |              |
|---------------|--------------|--------------|
|               | R1-L vs Ex L | R2-L vs Ex L |
| Percent Error | 85.5%        | 2.1%         |
| t-value       | -234.5       | 6.129        |

The result of the  $L_1$  shows a great difference on t-value and percent error with the labeled value. Therefore, in this case, I cannot prove the dependence of  $\tau$  on R according to Equation 5. However, I do not think that this is because of the lack of accuracy or calculation error. I speculate this as a random error from the data collected with resistor 100 ohms. Prior to taking the measurement, the device failed to deliver the expected result several times. Both TA's came to help and spent a lot of time trying to get the machine to work.

- Derive relationship between steady state voltage ( $t \gg \tau$ ) of the inductor and the resistances in the circuit (as well as the applied voltage). Calculate values for the voltage for both resistors.

According to Ohm's Law:  $I_{max} = \frac{V}{R_{total}}$

$$V_{steady,L} = V_0 - V_R = V_0 - IR_r$$

Therefore

$$V_{steady,L} = V_0 - \frac{V}{R_{total}} R_r = \frac{V_0 R_L}{R_r + R_L}$$

For Resistor 1:

$$V_0 = 1 \quad V_{steady,L} = 0.628$$

For Resistor 2:

$$V_0 = 1 \quad V_{steady,L} = 0.300$$

Error of Propagation:

$$\partial V_{steady,L} = \sqrt{\left( \left( \frac{V_0}{(R_r + R_L)} - \frac{V_0 R_L}{(R_r + R_L)^2} \right) \times \partial R_L \right)^2 + \left( -\frac{V_0 R_L}{(R_r + R_L)^2} \times \partial R_r \right)^2}$$

Voltage of Resistor 1: 0.628± 0.001 V

Voltage of Resistor 2: 0.300± 0.001 V



- Determine steady state voltage from both plots fitted parameters and verify the expected values.

Voltage of measured Resistor 1 (100 ohms):  $0.3427 \pm 0.0001$

Voltage of Resistor 2(330 ohms):  $0.3378 \pm 0.0001$

|         |         |         |
|---------|---------|---------|
|         | V of R1 | V of R2 |
| %Error  | 83.3%   | 11.2%   |
| t-value | 264.9   | 37.6    |

See note of Analysis Section 5.1 Question 5.

### Section 7

- Determine  $\tau$  values from fitted parameters (with/without core).

From Eq (5) and its error of propagation in Analysis Section 5.1 second question:

No core  $0.000510 \pm 0.000001$

With core:  $0.00208 \pm 0.00001$

- Determine the inductance values (with and without core)

|                          | With Iron Core        | Without Iron Core    |
|--------------------------|-----------------------|----------------------|
| Resistor (330 $\Omega$ ) | $323.7 \pm 5.5$       | $323.7 \pm 5.5$      |
| Resistance(In)           | $5.5 \pm 0.1$         | $5.5 \pm 0.1$        |
| Resistance (tot)         | $329.2 \pm 0.2$       | $329.2 \pm 0.2$      |
| Inductance (In)          | $0.0211 \pm 0.1$      | $0.0081 \pm 0.1$     |
| $\tau$                   | $0.000641 \pm 0.0003$ | $0.00246 \pm 0.0003$ |

### 6. Discussion

Yes, the inductance value is different than in the absence of the iron core. The iron core has a stronger magnetic field that induces the inductor even more, hence the increase of inductance. The change of magnetic field passing through the solenoid induces a voltage, hence the inductance. The inductance is directly proportional to the magnetic flux. Eq(2) shows that the magnetic flux is directly proportional to the cross-sectional area of the inductor. The greater the area, the more inductance. It is also correlates to the number of turns in the wire. The more turns in wire the more inductance. Also the shorter the time is spent on the same magnetic flux the greater inductance. This suggests the origin of the inductance is based on the circuits components such as the wire and the nature of the inductor, these directly affect the magnetic flux and the inductance.